


Chapter 4

HDL Coding Style

Outline

- ◆ **HDL and Synthesis Concept**
- ◆ Hierarchy of HDL design
- ◆ Latch inference and registers
- ◆ Instantiation and Black box
- ◆ Synchronous and Asynchronous Design
- ◆ Combinatorial and Sequential Logic
- ◆ Case V.S. If - elsif
- ◆ Others


Language Subsets

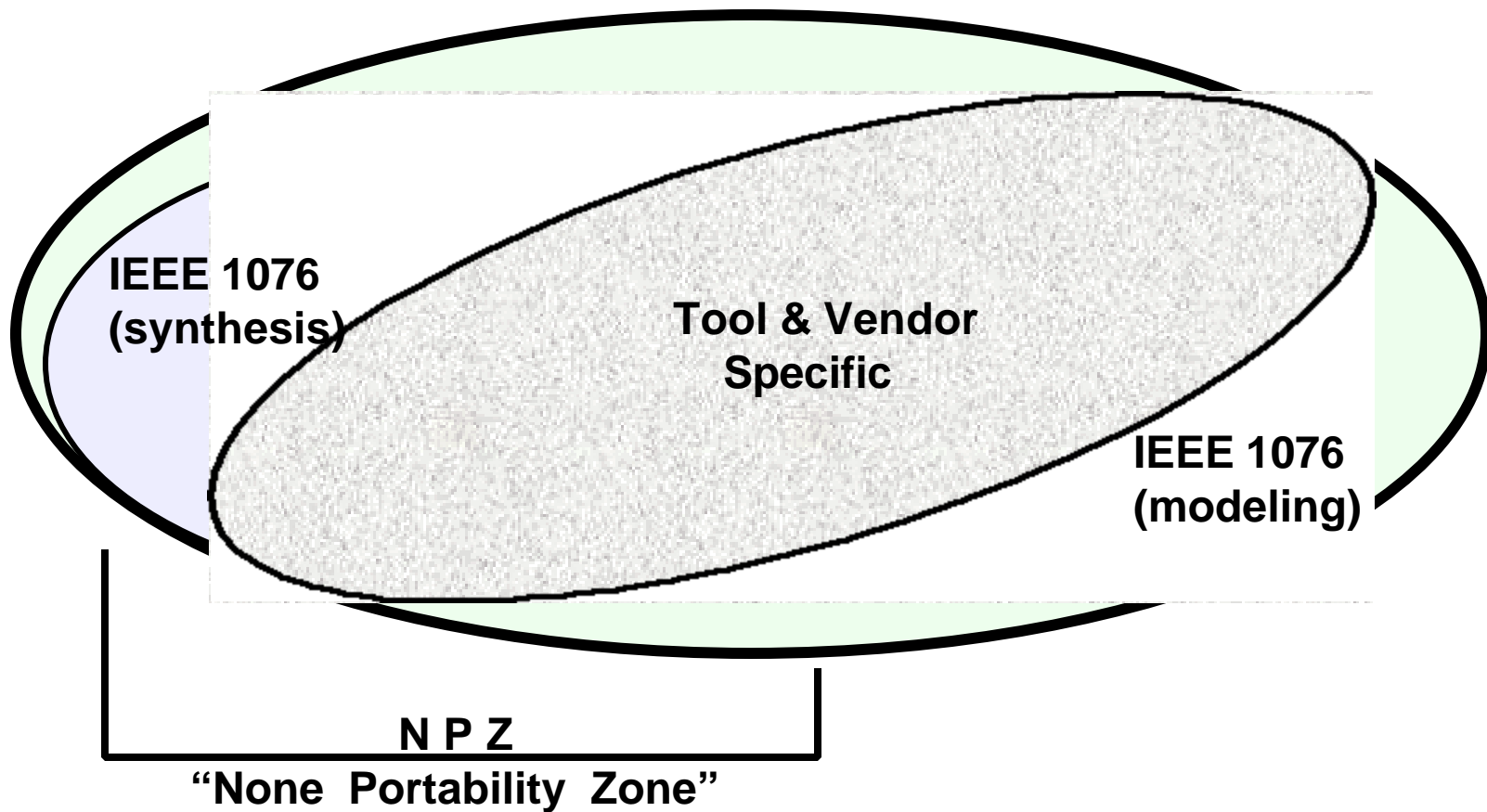

Avoid extensive use of tool specific constructs
that are outside of standard VHDL



Design Verification

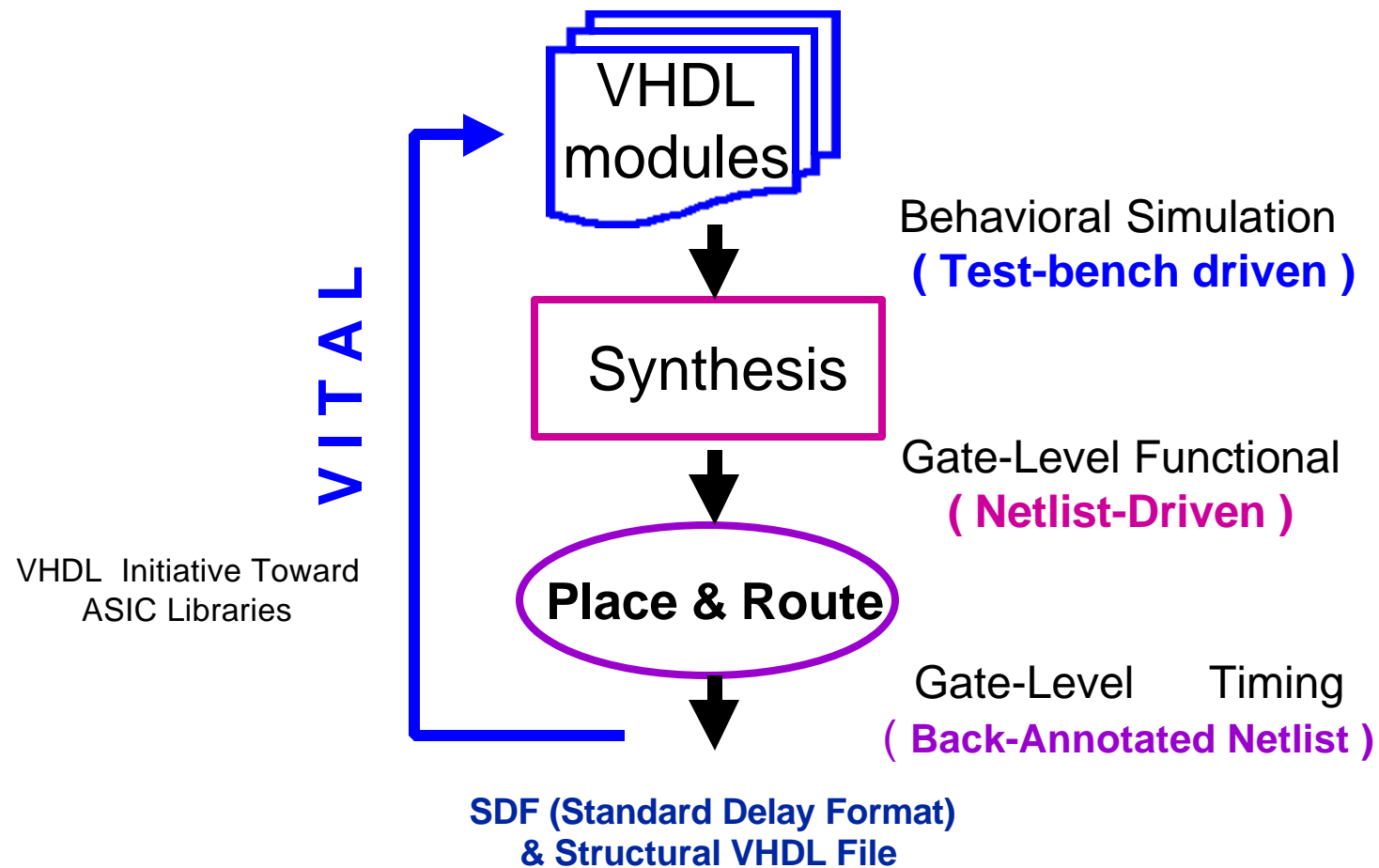- When using an HDL entry method, there is an additional level of design verification available.



Technology Independent Synthesis

  - ◆ The synthesis process consists of two steps:
 - ❶ **Synthesis** technology & constraint independent
 - ❷ **Optimization** technology & constraint driven
- ◆ Decisions made at the synthesis stage have effect on implementation
 - this is where your HDL coding style has an impact
- ◆ Take a simple example: a 16-to-1 multiplexer...



```
-- 4 to 1 multiplexer design with case construct  
--      SEL: in STD_LOGIC_VECTOR(1 downto 0);  
--      A, B, C, D:in STD_LOGIC;  
--      MUX_OUT: out STD_LOGIC;
```

```
process (SEL, A, B, C, D)  
begin  
    case SEL is  
        when "00" => MUX_OUT <= A;  
        when "01" => MUX_OUT <= B;  
        when "10" => MUX_OUT <= C;  
        when "11" => MUX_OUT <= D;  
    end case;  
end process;
```

```
-- 4 to 1 multiplexer design with tri-state construct  
--     SEL: in STD_LOGIC_VECTOR(3 downto 0);  
--     A, B, C, D:in STD_LOGIC;  
--     MUX_OUT: out STD_LOGIC;
```


```
MUX_OUT <= A when (SEL(0)='0') else 'Z';  
MUX_OUT <= B when (SEL(1)='0') else 'Z';  
MUX_OUT <= C when (SEL(2)='0') else 'Z';  
MUX_OUT <= D when (SEL(3)='0') else 'Z';
```

Outline

- ◆ HDL and Synthesis Concept
- ◆ **Hierarchy of HDL design**
- ◆ Latch inference and registers
- ◆ Instantiation and Black box
- ◆ Synchronous and Asynchronous Design
- ◆ Combinatorial and Sequential Logic
- ◆ Case V.S. If - elsif
- ◆ Others

Using Hierarchy in HDL

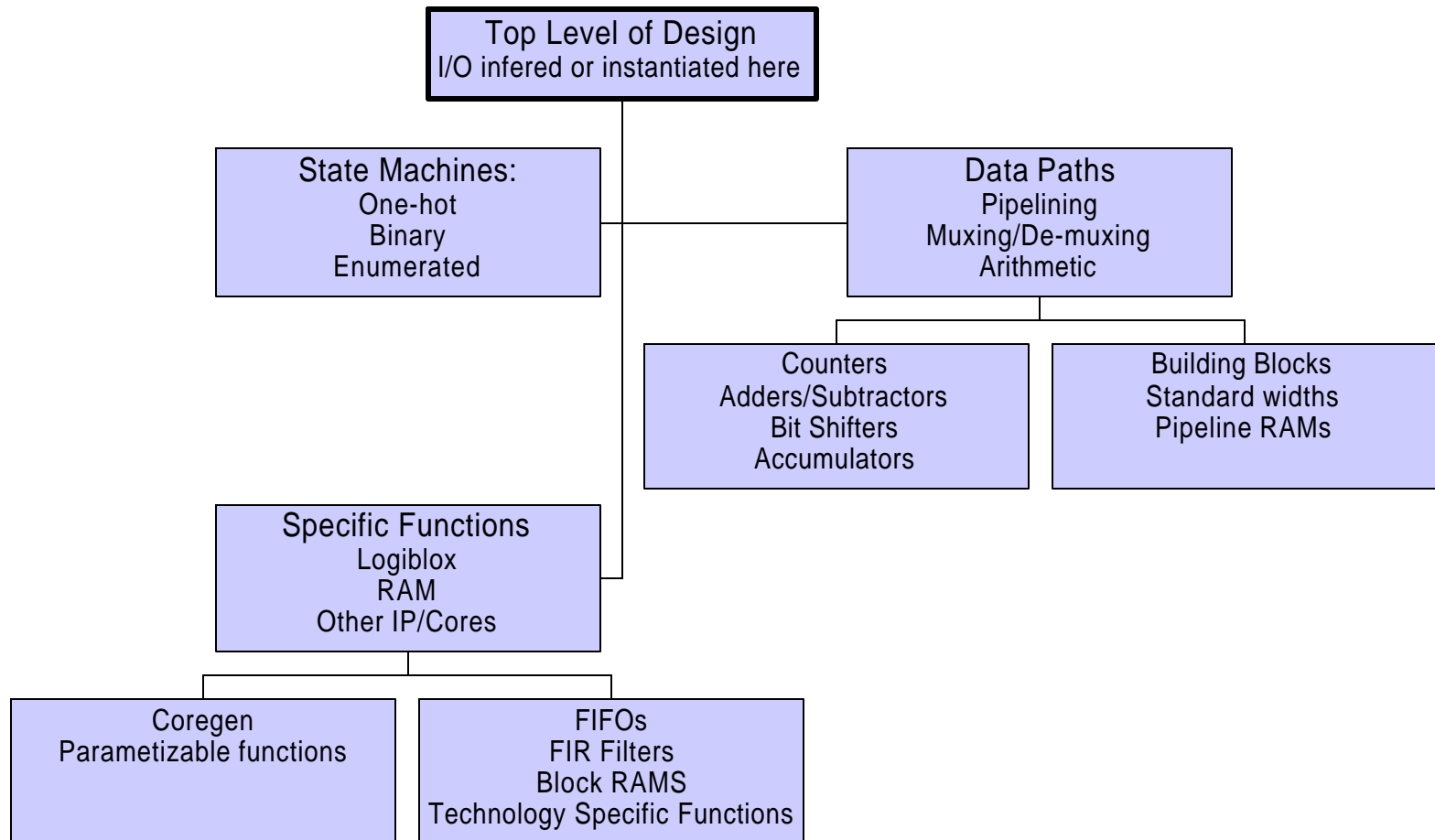- ◆ **Using Hierarchy** leads to easy design readability, re-use, and debug




Guidelines for Choosing Hierarchy

- ◆ Consider the following points when arranging your hierarchy
 - all **arithmetic operators** should be evaluated for resource sharing and combined within the same hierarchy/process
 - keep distinct **logic-types** (such as state machines, random logic, data paths, etc.) separate, so the appropriate optimizations can be applied to each
- ◆ Choose modules that have
 - a minimum of routing between modules
 - a logical data flow between modules
- ◆ Some synthesis tools flatten the design before optimization
- ◆ There are commands to remove hierarchy
 - in general, leave hierarchy in the design for later visibility into the design after place and route

Keep Related Logic Together (1)

No Hierarchy in Combinational Path

 
- The path from Reg A to Reg C is divided between three different block descriptions



- Example - Optimization is limited because hierarchical boundaries prevent sharing of common terms

Keep Related Logic Together (2)


Good Example

 

- **Related combinational** logic drive registers in the same block
- **No hierarchical boundaries between combinational logic and registers**
 - **Allows for improved sequential mapping**

Register Hierarchical Boundaries

 
- ◆ This reduces the amount of cross boundary optimization the synthesizer must do
- ◆ **(X) Bad Module Boundary:**



At this boundary, the Synthesis tool must decide how much to optimize Logic B and C together? It is un-wise to let the synthesis tool make a judgement call about your design. **This type of design leads to bigger, slower**, and less likely to work designs

Register Hierarchical Boundaries

 - ◆ Register Boundary at the output of each module provides a more stable, re-useable, and synthesizable design
- ◆ **Good Module Boundary:**



At this boundary, the Synthesis tool has no decisions to make. **Logic B is going to be synthesized the same every time**, regardless of which module is attached to its inputs or outputs. Additionally, Module 2 can be synthesized and tested on its own, to insure performance as expected.

Use Hierarchy to Isolate Technology

- ◆ **Put technology specific cores in their own hierarchical blocks to allow for maximum design re-use**
 - Xilinx block RAMs, distributed RAMs, DLLs, I/Os, clock buffers, global resets, Coregen modules
- ◆ **Keep clock domains separated by using hierarchy**
 - this makes the interaction between clocks very clear in the design
 - reduces un-wanted clock confusion
 - easier to add timing constraints later
 - allows different design section to be synthesized individually, and tested before they are part of the larger design
- ◆ **Keep the number of lines of code per module below 400**
 - the modules are easier to read
 - the modules are easier to debug and synthesize.

Use Hierarchy to make Design Building Blocks

- ◆ Build yourself a standard set of functions you can re-use throughout your design
 - muxes, register banks, FIFOs, adders, counters, and other standard functions
- ◆ **Compile from the bottom up**
 - synthesize each low level module on it own the first time
 - run these lower levels into the Xilinx tools to get a resource usage estimate for each module and design sub-section
 - **be sure each sub-block can meet your requirements before adding it into the main design**: Is it the right size? Is it fast enough?

Outline

- ◆ HDL and Synthesis Concept
- ◆ Hierarchy of HDL design
- ◆ **Latch inference and registers**
- ◆ Instantiation and Black box
- ◆ Synchronous and Asynchronous Design
- ◆ Combinatorial and Sequential Logic
- ◆ Case V.S. If - elsif
- ◆ Others

Watch for Unintentional Latches

- ◆ Completely specify all clauses for every case and if statement
- ◆ Completely specify all outputs for every case or if statement: Unspecified outputs are required to retain their old values
- ◆ Elaboration will report all generated registers

What's wrong with these example coding sections?

```
process (A, B) begin
    if (A = '1') then
        Q <= B;
    end if;
end process;
```

(Latch Inferred)

```
process (C) begin
    case C is
        when '0' => Q <= '1';
        Z <= '0';
        when others => Q <= '0';
    end case;
end process;
```

(Missing Z Output)

(Missing Case)

(Missing Outputs)

```
always @ (D) begin
    case (D)
        2'b00: Z = 1'b1;
        2'b01: Z = 1'b0;
        2'b10: S = 1'b1;
    endcase
end
```

Verilog

Implementing Registers (VHDL)

◆ D Flip Flop

```
FF: process (CLK)
begin
    if (CLK'event and CLK='1') then
        Q <= D_IN;
    end if;
end process
```

◆ Flip-Flop with async. reset

```
FF_AR: process(RESET,CLOCK)
begin
    if (RESET = '1') then
        Q <= '0';
    elsif (CLK'event and CLK='1') then
        Q <= D_IN;
    end if;
end process
```

◆ Flip-Flop with async. set

```
FF_AS: process(RESET,CLOCK)
begin
    if (RESET = '1') then
        Q <= '1';
    elsif (CLK'event and CLK='1') then
        Q <= D_IN;
    end if;
end process
```

◆ Flip-Flop with sync. set

```
FF_SS: process(CLOCK)
begin
    if (CLOCK'event and CLOCK='1') then
        if (RESET = '1') then
            Q <= '0';
        else
            Q <= D_IN;
        end if;
    end if;
end process
```

Instantiation

- ◆ Instantiation is how you dictate to a synthesis tool that you want to use a specific component from the Xilinx library
- ◆ **Instantiation makes your HDL code vendor specific**, and can make behavioral simulation difficult
- ◆ Certain Xilinx functions can only be activated by instantiation
 - Clock buffers/DLL Unbonded pads
 - Boundary scan All types of RAM modules
 - Start-up block Virtex Select I/O
- ◆ Instantiated components might need a *don't touch* or *black box* attribute to prevent them from being changed or removed by the synthesis tool

Using Black Boxes

- ◆ Sometimes Black Boxes Need to be Instantiated:
 - RAM and ROM
 - IP Cores (PCI, DSP, etc.)
 - Other Hard Macros
- ◆ Black Boxes are Empty Placeholders in the Design Hierarchy
- ◆ Black Box Functions are Linked by the Place & Route Tool

Using Black Boxes

VHDL Requires a Component Declaration for the Port Directions

```
component MY_BLACK_BOX
  port(a, b: in std_logic; y, z: out std_logic);
end component;

...

u1: MY_BLACK_BOX
  port map(a => a_int, b => b_int,
    y => y_int, z => z_int);
```



Verilog Requires an Empty Module Definition for the Port Directions

```
module top(
  ...
  MY_BLACK_BOX u1(.a(a_int), .b(b_int),
    .y(y_int), .z(z_int));
  ...
endmodule

module MY_BLACK_BOX(a, b, y, z);
input a, b;
output y, z;
endmodule
```

Think Synchronous Hardware

  - ♦ *Synchronous* designs run smoothly through synthesis, simulation and place & route.
- ♦ *Asynchronous* designs may require instantiation and placement to verify. If asynchronous logic is necessary, isolate into separate blocks.




**Asynchronous
Address
Decoder**

**How am I going to
synthesize this?**

Think RTL Description of Synchronous Hardware

 - Describe the register-to-register functionality of the design (i.e., describe the function of the combinational logic *between* registers).



```
module GIZMO (A, CLK, Z);  
...  
always@ (A) begin : COMBO1...  
always@ (posedge CLK)...  
always@ (B) begin : COMBO2...  
always@ (posedge CLK) ...  
end module;
```

```
entity GIZMO is  
...  
architecture RTL of GIZMO is  
begin  
    COMBO1 : process (A) ...  
    REG1 : process (CLK) ...  
    COMBO2 : process (B) ...  
    REG2 : process (CLK) ...  
end RTL;
```


Separate Combinational from Sequential

- Easy to read and “self-documenting”
- Follows RTL coding style.


```

module EXAMPLE (DATA1,DATA2,CLK,Q)
input DATA1,DATA2,CLK;
output Q;
reg DATA, Q;

always @ (DATA1 or DATA2)
  begin: COMBO
    DATA = GOBBLEDYGOOK (DATA1,DATA2);
  end

always @ (posedge CLK)
  begin: SEQUENTIAL
    Q <= DATA;
  end
endmodule

```

 

```

library IEEE;
use IEEE.std_logic_1164.all;

entity EXAMPLE is
port (DATA1,DATA2,CLK: in STD_LOGIC;
      Q: out STD_LOGIC);
end EXAMPLE;

architecture SEPARATE of EXAMPLE is
signal DATA: STD_LOGIC_VECTOR(7 downto 0);
begin
  COMBO: process (DATA1, DATA2) begin
    DATA <= GOBBLEDYGOOK (DATA1, DATA2);
  end process COMBO;

  SEQUENTIAL: process (CLK) begin
    if (CLK'EVENT and CLK = '1') then
      Q <= DATA;
    end if;
  end process SEQUENTIAL;
end SEPARATE

```

Clock Enable Coding

- ◆ Coding Style will determine if clock enables are used
- ◆ Makes timing constraints easier to control

- VHDL

```
FF_AR_CE: process(RESET,CLK)
begin
  if (RESET = '1') then
    Q <= '0'
  elsif (CLK'event and CLK='1') then
    if (ENABLE = '1') then
      Q <= D_IN;
    end if;
  end if;
end process
```


- Verilog

```
always @(posedge CLOCK or posedge RESET)
  if (RESET)
    Q = 0;
  else if (ENABLE)
    Q = D_IN;
```

Combinatorial Logic: Say what you mean


- ◆ Parentheses to control logical structure
 
```
-- No parentheses  
OUT1 <= I1 + I2 + I3 + I4
```



3 Layers of Logic
 
```
-- With parentheses  
OUT1 <= (I1 + I2) + (I3 + I4)
```



2 Layers of Logic

Combinatorial Logic: Say what you mean

- ◆ Don't use a process (VHDL) or always block (Verilog) when a **concurrent assignment** can be used.

Verilog

```
Always @ (A or B or C)
begin
    if(A)
        Y = C;
    else
        Y = B;
end
```

VHDL

```
Process(A,B,C)
begin
    if (A = '1') then
        Y <= C;
    else
        Y <= B;
    end if;
end process;
```

A Better way...

$Y \leq A ? C : B;$

$Y \leq C \text{ when } A = '1' \text{ else } B;$

Synthesis of **if-then-elsif** Statement

- ♦ if-then-elsif statements *imply* priority-encoded MUXs.


```
process (SEL, A,B,C,D) begin
  if (SEL(2) = '1') then
    OUTI <= A;
  elsif (SEL(1) = '1') then
    OUTI <= B;
  elsif (SEL(0) = '1') then
    OUTI <= C;
  else
    OUTI <= D;
  end if;
end process;
```

VHDL Code

```
always@ (SEL or A or B or C or D)
  if (SEL[2] == 1'b1)
    OUTI = A;
  else if (SEL[1] == 1'b1)
    OUTI = B;
  else if (SEL[0] == 1'b1)
    OUTI = C;
  else
    OUTI = D;
```

Verilog Code

Hardware Result

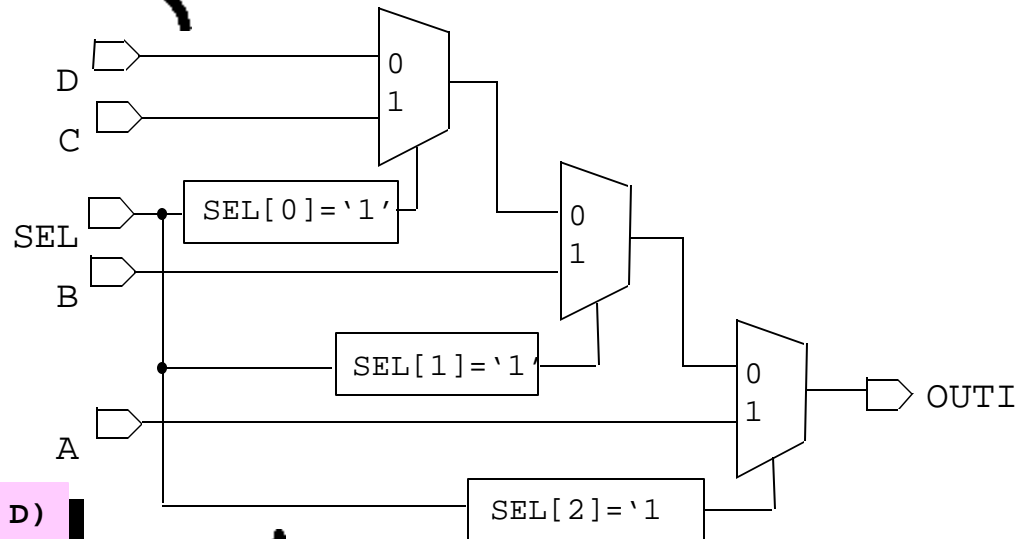


Critical Inputs in IF/ELSE Statements

◆ Fast critical signals

```
IF critical_signal THEN do_a  
  ELSIF cond_b THEN do_b  
  ELSIF cond_c THEN do_c  
  ELSIF cond_d THEN do_d  
  ELSE do_e  
END IF;
```

◆ Slows down critical signals
 
```
IF cond_b THEN do_b  
  ELSIF cond_c THEN do_c  
  ELSIF cond_d THEN do_d  
  ELSIF critical_signal THEN do_a  
  ELSE do_e  
END IF;
```



Case Statements I

- ◆ All branches of a case statement must be defined
 - enumerated states can all be defined
 - std_logic_vector has several more values than '0' or '1'
- ◆ If there are conditions that have "don't care", set output values to:
 - VHDL: Pick '1' or '0' based on logic reduction or '-' (**don't care**) for std_logic
 - Verilog: use don't care value ex: 1'bX
- ◆ Avoid using ranges in your HDL code - creates comparitors
case COUNTER is
 when 0 to 9 =>
 display <= SEVEN_SEG(COUNTER);
- ◆ Use explicit numbers - creates a decoder
case COUNTER is
 when 0!1!2!3!4!5!6!7!8!9 =>
 DISPLAY <= SEVEN_SEG(COUNTER)

Case Statements II

- ◆ Case statements in combinatorial process(VHDL) or always statement (Verilog):
 - **all outputs must be defined in all branches** of the case statement to **prevent latches**.
 - use a default statement before case statement to prevent latches
- ◆ Case statements in sequential process(VHDL) or always statement (Verilog):
 - clock enables generated if outputs are not defined in all branches
 - this is not “wrong”, but might generate a long clock enable equation
 - use a default statement before case statement to prevent clock enables

Synthesis of case Statement


- ◆ Case statements *imply* parallel mux function.

```
process (SEL,A,B,C,D) begin
  case SEL is
    when "00" => OUTC <= A;
    when "01" => OUTC <= B;
    when "10" => OUTC <= C;
    when others => OUTC <= D;
  end case;
end process;
```

VHDL Code

```
always@(SEL or A or B or C or D)
begin
  case (SEL)
    2'b00 : OUTC = A;
    2'b01 : OUTC = B;
    2'b10 : OUTC = C;
    default : OUTC = D;
  endcase
end
```

Verilog Code

 

Arithmetic Operators

- ◆ Operators Inferred from HDL
 - Adder, Subtractor, AddSub (+, -)
 - Multiplier (*)
 - Comparators (>, >=, <, <=, =, /=)
 - Incrementer, Decrementer, Incdec (+1, -1)
 - Counters

Magnitude Compare

- ◆ This can be done as subtractor with sign extension on the inputs. Below is $A > B$, reverse the subtraction to get $A < B$
- ◆ The subtractor will be created using the carry chain inside the FPGA, **writing $A > B$ in your code will be Bigger & Slower**

Verilog:

```
wire [7:0] A, B;
reg  [8:0] A_ext, B_ext;
reg  [8:0] sub;
reg          mag_comp;

always@(A or B)
begin
    A_ext <= {A(7),A};
    B_ext <= {B(7),B};
    sub   <= A_ext - B_ext;
    mag_comp <= sub(8);
end
```


VHDL:

```
signal A:      std_logic_vector (7 downto 0);
signal B:      std_logic_vector (7 downto 0);
signal A_ext: std_logic_vector (8 downto 0);
signal B_ext: std_logic_vector (8 downto 0);
signal sub:    std_logic_vector (8 downto 0);
signal mag_comp: std_logic;


process (A, B) begin
    A_ext <= (A(7)&A);
    B_ext <= (B(7)&B);
    sub   <= A_ext - B_ext;
    mag_comp <= sub(8);
end process;
```

Operator Balancing

- ◆ Depends on parenthesis

 

$(A * B) * (C * D)$

 


$A * B * C * D$

Sharing of Arithmetic Operators


- ◆ Operators can be Shared Within:
 - - A Process (VHDL)
 - - An *always* Block (Verilog)

```
process (S,A,B,C)
begin
  if (S) then
    Z <= A+B;
  else
    Z <= A+C;
  end if;
end process;
```

With Sharing

 


Without Sharing

 

FSM Encoding

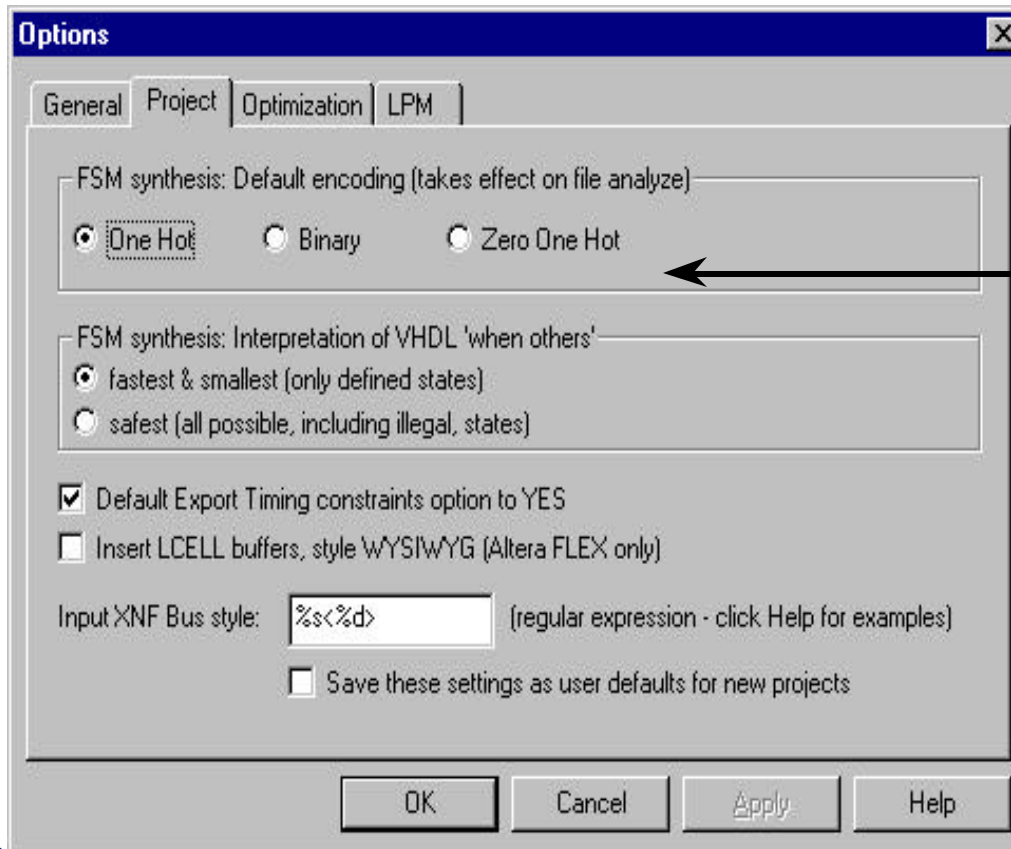- ◆ FPGA Express: manual extraction and re-encoding using FSM Compiler



**You can choose one-hot,
binary, or zero one-hot
encoding**

VHDL: Avoid Integers

- ◆ Integers are 32 bits wide
- ◆ Integer Types Default to Signed
- ◆ Use constrained `std_logic_vector` instead
 - e.g. `std_logic_vector(7 downto 0)`
 - include arithmetic packages:
 - `ieee.std_logic_unsigned.all`
 - `ieee.std_logic_signed.all`

Synopsys Translation Directives

- ◆ Useful for ignoring simulation constructs
- ◆ VHDL
 - `-- pragma translate_off` or `-- synopsys translate_off` to start
 - `-- pragma translate_on` or `-- synopsys translate_on` to finish
 - use `synthesis_off/synthesis_on` to check ignored code for syntax
- ◆ Verilog
 - `// synopsys translate_off` to start
 - `// synopsys translate_on` to finish
 - Turn Verilog Pre-Processor (VPP) ON to use `'ifdef`

How to implement a Synchronous Reset

- ◆ This must be declared at the top of the VHDL file as shown:
`library synopsys;`
`use synopsys.attributes.all;`
- ◆ Then attach the "`sync_set_reset`" attribute to the reset signal.
- ◆ Here is the section of VHDL code that will infer the synchronous reset:

`attribute sync_set_reset of RESET: signal is "true";`

VHDL Example

```
library synopsys;
```

```
use synopsys.attributes.all;
```

```
....
```

```
architecture COUNT_ARCH of COUNTER is
```

```
    signal COUNT: STD_LOGIC_VECTOR (7 downto 0);
```

```
    attribute sync_set_reset of RESET: signal is "true";
```

```
begin
```

```
process (CLK, RESET)
```

```
begin
```

```
if (CLK'event and CLK='1') then
```

```
    if (RESET='1') then
```

```
        COUNT <= "00000000";
```

```
    else
```

```
        COUNT <= COUNT + 1;
```

```
    end if;
```

```
end if;
```

```
end process;
```

Verilog Example

- ◆ No library needs to be defined for Verilog.

```
//synopsys sync_set_reset "RESET"
```

```
always @(posedge CLK)
  if (RESET)
    COUNT = 8'b00000000;
  else
    COUNT = COUNT + 1;
```